

## 2. Transmission line theory

22

Maxwell's eqs. (see p.14 (50)(51), p8 (24))

$$\left\{ \begin{array}{l} \nabla \times \mathbf{E} = -j\omega\mu \mathbf{H} - \sigma_m \mathbf{H} = -j\omega\mu \left(1 + \frac{\sigma_m}{j\omega\mu}\right) \mathbf{H} \\ \nabla \times \mathbf{H} = j\omega\epsilon \mathbf{E} + \sigma \mathbf{E} = j\omega\epsilon \left(1 + \frac{\sigma}{j\omega\epsilon}\right) \mathbf{E} \end{array} \right. \quad (70) \quad (71)$$

Wave number

$$k^2 = \omega^2 \mu \epsilon \quad \xrightarrow{\text{replaced by}} \quad \omega^2 \mu \epsilon \left(1 - j \frac{\sigma_m}{\omega\mu}\right) \left(1 - j \frac{\sigma}{\omega\epsilon}\right)$$

$$\text{or,} \quad k = \omega \sqrt{\mu \epsilon} \sqrt{\left(1 - j \frac{\sigma_m}{\omega\mu}\right) \left(1 - j \frac{\sigma}{\omega\epsilon}\right)} \quad (72)$$

$$\text{Complex propagation constant } \gamma = \alpha + j\beta = jk = j\omega \sqrt{\mu \epsilon} \sqrt{\left(1 - j \frac{\sigma_m}{\omega\mu}\right) \left(1 - j \frac{\sigma}{\omega\epsilon}\right)} \quad (73)$$

Similar discussion in the case of a transmission line

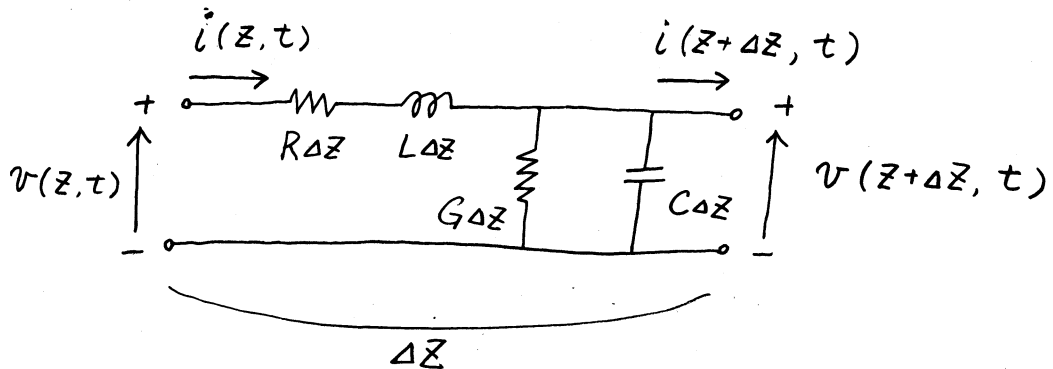


Fig. equivalent circuit for an incremental length of transmission line

Q. What is the relation between  $v$  and  $i$  ?

$$\left\{ \begin{array}{l} \frac{\partial v(z,t)}{\partial z} = -R i(z,t) - L \frac{\partial i(z,t)}{\partial t} \quad (74) \\ \frac{\partial i(z,t)}{\partial z} = -G v(z,t) - C \frac{\partial v(z,t)}{\partial t} \quad (75) \end{array} \right.$$

or in the phasor form,  $v = \text{Re}[V e^{j\omega t}]$ ,  $i = \text{Re}[I e^{j\omega t}]$

$$\left\{ \begin{array}{l} \frac{dV(z)}{dz} = -(R + j\omega L) I(z) \quad (76) \\ \frac{dI(z)}{dz} = -(G + j\omega C) V(z) \quad (77) \end{array} \right.$$

↓ comparison with (70) and (71)

• the complex propagation constant

$$\begin{aligned} \gamma & (= jk = j\sqrt{\omega^2 \epsilon \mu}) \\ & (= \alpha + j\beta) \\ & = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (78) \end{aligned}$$

equivalent to the 1D Maxwell's equations

• the characteristic impedance

$$Z_0 \left( = \sqrt{\frac{\mu}{\epsilon}} \right) = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} \quad (79)$$

Q. Derive a wave equation from (76) and (77) to get (78).

Ans. 
$$\begin{aligned} \frac{d^2 V}{dz^2} &= -(R + j\omega L) \frac{dI}{dz} \\ &= (R + j\omega L)(G + j\omega C) V \end{aligned}$$

$$\therefore \frac{d^2 V}{dz^2} - \gamma^2 V = 0, \text{ where } \gamma^2 = (R + j\omega L)(G + j\omega C) //$$

Q. Obtain the propagation constant  $\gamma = \alpha + j\beta$  and the characteristic impedance  $Z_0$  for the lossless line ( $R=G=0$ ). Use (78) and (79).

The solution to (76) and (77) is expressed as

$$\begin{cases} V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} & (80) \\ I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} & (81) \end{cases}$$

Q. Apply (76) to (79) to get the current on the line.

$$\begin{aligned} I(z) &= \frac{1}{-(R + j\omega L)} [-\gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{\gamma z}] \\ &= \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z}, \end{aligned} \quad (82)$$

$$\text{where } Z_0 = \frac{R + j\omega L}{\gamma}$$

$$= \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} \quad (83)$$

## Terminated line

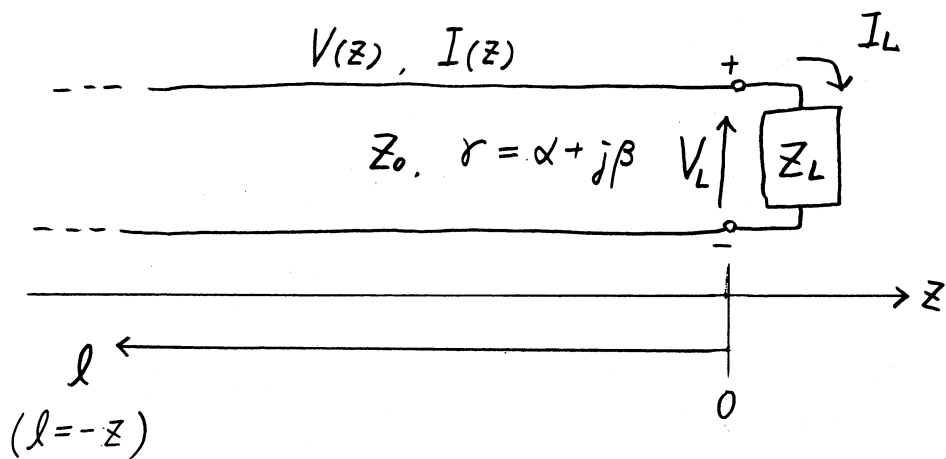


Fig. A terminated transmission line.

The total voltage on the line (sum of incident and reflected wave)

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}, \quad (84)$$

and the total current: (82)

$$I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z} \quad (85)$$

The load (\$Z\_L\$) condition:

$$\begin{aligned} Z_L = \frac{V_L}{I_L} &= \frac{V(0)}{I(0)} = \frac{V_0^+ + V_0^-}{\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}} \\ &= Z_0 \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \end{aligned} \quad (86)$$

solving (85) for \$V\_0^-\$ gives

$$V_0^- = \frac{Z_L - Z_0}{Z_L + Z_0} V_0^+ \equiv \Gamma V_0^+ \quad (87)$$

$$\Gamma \equiv \frac{V_0^-}{V_0^+} : \text{voltage reflection ratio}$$

Ex. How large is the reflected voltage in the following case? Also in dB?



$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R_L - Z_0}{R_L + Z_0} = \frac{100 - 50}{100 + 50} = \frac{50}{150} = 0.333\ldots \quad (88)$$

$$[\text{dB}] = -20 \log_{10} \Gamma = -20 \times (-0.477) \approx 9.54 \text{ dB}$$

Conversion between  $\Gamma$  and  $Z_L$


From (87)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (87a)$$




$$\Gamma(Z_L + Z_0) = Z_L - Z_0$$
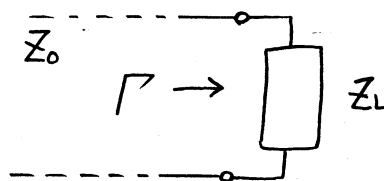
$$Z_L = Z_0 \frac{1 + \Gamma}{1 - \Gamma} \quad (87b)$$



Note:  $Z_0, Z_L, \Gamma$ : complex numbers

Fig (p.25)

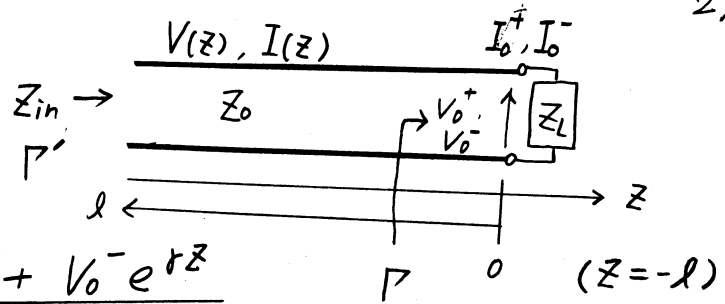

$$\begin{aligned}
 Z_{in} &= \frac{V(z)}{I(z)} \\
 &= \frac{V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}}{\frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z}} \\
 &= Z_0 \cdot \frac{V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}}{V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}} \\
 &= Z_0 \cdot \frac{e^{-\gamma z} + (V_0^-/V_0^+) e^{\gamma z}}{e^{-\gamma z} - (V_0^-/V_0^+) e^{\gamma z}} \\
 &= Z_0 \cdot \frac{e^{-\gamma z} + \Gamma e^{\gamma z}}{e^{-\gamma z} - \Gamma e^{\gamma z}} = Z_0 \frac{1 + \Gamma e^{2\gamma z}}{1 - \Gamma e^{2\gamma z}} \quad (*)
 \end{aligned}$$

Now we know that

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (88)$$

$\uparrow \Gamma' = \Gamma e^{2\gamma z}$   
 $= \Gamma e^{-2\gamma l}$

therefore,

$$\begin{aligned}
 Z_{in} &= Z_0 \frac{(Z_L + Z_0) e^{-\gamma z} + (Z_L - Z_0) e^{\gamma z}}{(Z_L + Z_0) e^{-\gamma z} - (Z_L - Z_0) e^{\gamma z}} \\
 &= Z_0 \frac{Z_L (e^{-\gamma z} + e^{\gamma z}) + Z_0 (e^{-\gamma z} - e^{\gamma z})}{Z_L (e^{-\gamma z} - e^{\gamma z}) + Z_0 (e^{-\gamma z} + e^{\gamma z})} \quad (89)
 \end{aligned}$$

Since Euler's identity is

$$\begin{cases} e^{\theta} = \cosh \theta + \sinh \theta \\ e^{-\theta} = \cosh \theta - \sinh \theta \end{cases} \quad \text{for } \theta: \text{ complex number. } (90)$$

$$\begin{aligned}
 Z_{in} &= Z_0 \frac{Z_L \cosh \gamma z + Z_0 (-\sinh \gamma z)}{Z_L (-\sinh \gamma z) + Z_0 \cosh \gamma z} \\
 &= Z_0 \frac{Z_L - Z_0 \tanh \gamma z}{Z_0 - Z_L \tanh \gamma z} \quad (\gamma = \alpha + j\beta) \quad (91)
 \end{aligned}$$

change the variable from  $Z$  to  $l$ , and consider (89) or (91) for lossless case

$$\begin{cases} \gamma = \alpha + j\beta \rightarrow j\beta \quad (\alpha=0) \\ e^{\gamma Z} \rightarrow e^{-\gamma l} \rightarrow e^{-j\beta l} \end{cases}$$

$$\begin{aligned} Z_{in} &= Z_0 \frac{Z_L (e^{j\beta l} + e^{-j\beta l}) + Z_0 (e^{j\beta l} - e^{-j\beta l})}{Z_L (e^{j\beta l} - e^{-j\beta l}) + Z_0 (e^{j\beta l} + e^{-j\beta l})} \\ &= Z_0 \frac{Z_L (\cos \beta l) + Z_0 (j \sin \beta l)}{Z_L (j \sin \beta l) + Z_0 (\cos \beta l)} \\ &= Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \quad \text{''} \end{aligned} \quad (92)$$

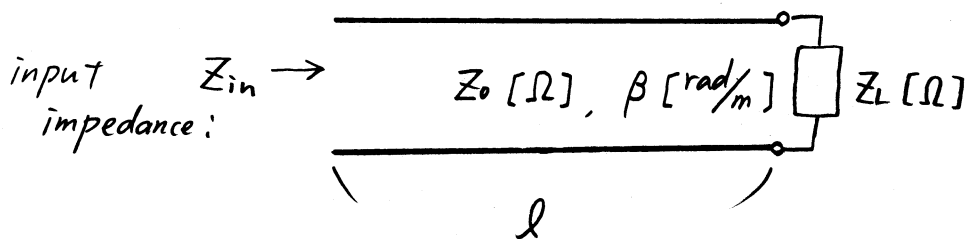


Fig. terminated lossless line

From (92),

short termination ( $Z_L = 0$ ) :  $Z_{in} = j Z_0 \tan \beta l$

open termination ( $Z_L = \infty$ ) :  $Z_{in} = -j Z_0 \cot \beta l$


half-wavelength line ( $l = \frac{\lambda}{2}$ ,  $\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi$ ) :  $Z_{in} = Z_L$

quarter-wavelength line ( $l = \frac{\lambda}{4}$ ,  $\beta l = \frac{\pi}{2}$ ) :  $Z_{in} = Z_0^2 / Z_L$

↓

quarter-wave transformer

## The Smith chart

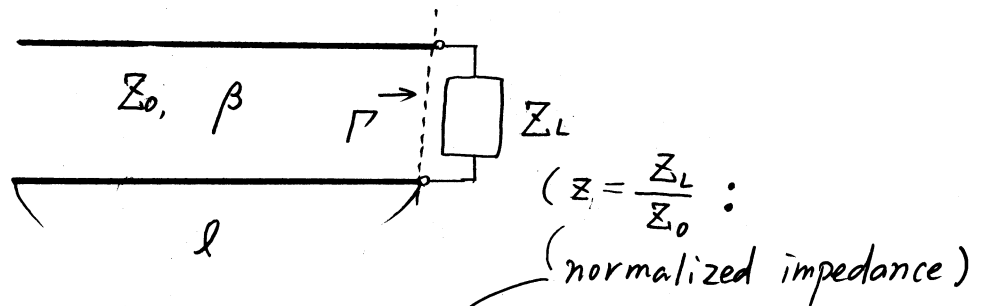

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z - 1}{z + 1} \quad (93)$$

Suppose the complex numbers :

$$\begin{cases} \Gamma = \Gamma_r + j\Gamma_i \\ z = r + jx \end{cases} \quad (94)$$

rewrite (93) as

$$\begin{aligned} (z+1)\Gamma &= z-1 \\ z(\Gamma-1) &= -(\Gamma+1) \\ z &= \frac{1+\Gamma}{1-\Gamma} \end{aligned} \quad (95)$$

substitute (94) into (95),

$$r + jx = \frac{(1+\Gamma_r) + j\Gamma_i}{(1-\Gamma_r) - j\Gamma_i} = \frac{\{(1+\Gamma_r) + j\Gamma_i\}\{(1-\Gamma_r) + j\Gamma_i\}}{\{(1-\Gamma_r) - j\Gamma_i\}\{(1-\Gamma_r) + j\Gamma_i\}}$$

$$r = \frac{(1+\Gamma_r)(1-\Gamma_r) - \Gamma_i^2}{(1-\Gamma_r)^2 + \Gamma_i^2}, \quad x = \frac{(1+\Gamma_r)\Gamma_i + \Gamma_i(1-\Gamma_r)}{(1-\Gamma_r)^2 + \Gamma_i^2}$$

$$= \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1-\Gamma_r)^2 + \Gamma_i^2}, \quad (96a) \quad = \frac{2\Gamma_i}{(1-\Gamma_r)^2 + \Gamma_i^2}, \quad (96b)$$



From (96a)

$$r(1-\Gamma_r)^2 + r\Gamma_i^2 = 1 - \Gamma_r^2 - \Gamma_i^2$$

$$r - 2r\Gamma_r + r\Gamma_r^2 + r\Gamma_i^2 = 1 - \Gamma_r^2 - \Gamma_i^2$$

$$(r+1)\Gamma_r^2 - 2r\Gamma_r + (r+1)\Gamma_i^2 + r - 1 = 0$$

$$\Gamma_r^2 - \frac{2r}{r+1}\Gamma_r + \Gamma_i^2 + \frac{r-1}{r+1} = 0$$

$$\left(\Gamma_r - \frac{r}{r+1}\right)^2 - \left(\frac{r}{r+1}\right)^2 + \Gamma_i^2 + \frac{r-1}{r+1} = 0$$

$$\left(\Gamma_r - \frac{r}{r+1}\right)^2 + \Gamma_i^2 - \frac{r^2}{(r+1)^2} + \frac{r^2-1}{(r+1)^2} = 0$$

$$\left(\Gamma_r - \frac{r}{r+1}\right)^2 + \Gamma_i^2 = \frac{1}{(r+1)^2}, \quad (97a)$$


which means a circle with center  $(\Gamma_r, \Gamma_i) = \left(\frac{r}{r+1}, 0\right)$ , and the radius  $\frac{1}{r+1}$ , and From (96b)

$$x(1-\Gamma_r)^2 + x\Gamma_i^2 = 2\Gamma_i$$


$$(\Gamma_r - 1)^2 + \Gamma_i^2 - \frac{2}{x}\Gamma_i = 0$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \frac{1}{x^2}, \quad (97b)$$

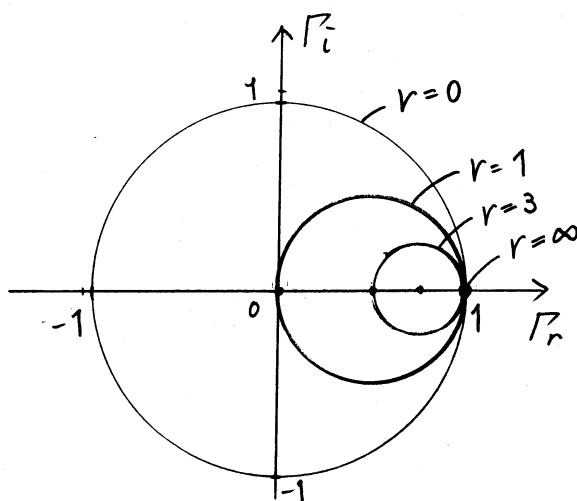which means a circle with center  $(\Gamma_r, \Gamma_i) = \left(1, \frac{1}{x}\right)$  and the radius  $\frac{1}{x}$ . Plotting the circles on  $\Gamma$  plane




(97a), constant- $r$  circles

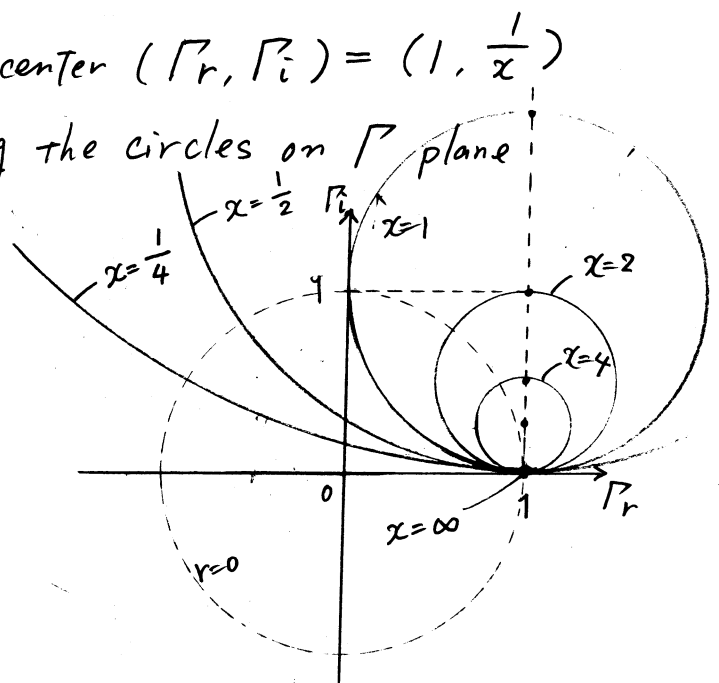

(97b) constant- $x$  circles

Ex. 1.

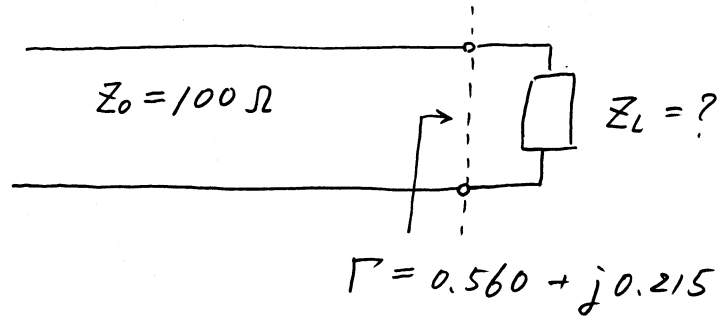

What's the load impedance ?

Ans.  $\Gamma = 0.560 + j0.215$   
 $= \sqrt{0.560^2 + 0.215^2} \angle \tan^{-1} \frac{0.215}{0.560}$   
 $= 0.6 \angle 21^\circ$

↓ plot on Smith chart,

$r = 2.6$ ,  $x = 1.8$


↓

$Z_L = 2.6 + j1.8$  (normalized impedance)

↓

$Z_L = Z_0 Z_L = 100 \cdot (2.6 + j1.8) = 260 + j180 \Omega$

Ex. 2

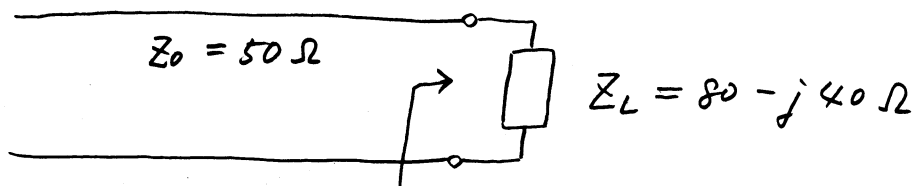

•  $\Gamma = ?$

• return loss [dB] = ?

• Standing wave ratio = ?

Ans.

$Z_L = \frac{Z_L}{Z_0} = 1.6 - j0.8$

↓

From Smith chart, we read that

$\Gamma = 0.36 \angle -36^\circ$

return loss = 8.7 dB, SWR = 2.1



# The Complete Smith Chart

Black Magic Design

$Z_0 = 100 \Omega$ ,  
 $Z_L = 2.6 + j1.8$

$Z_L = Z_0 z_L = 260 + j180 \Omega$



Ex. 1

$\Gamma = 0.560 + j0.215$

$= \sqrt{0.560^2 + 0.215^2}$

$\angle \tan^{-1} \frac{0.215}{0.560}$


$= 0.6 \angle 21^\circ$

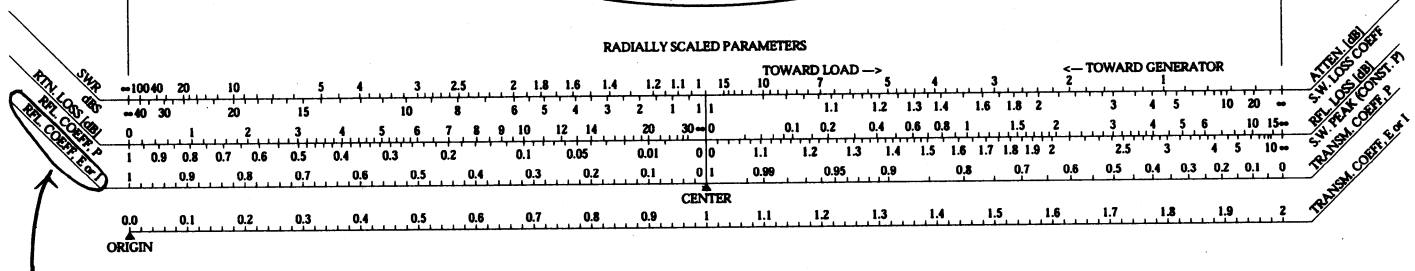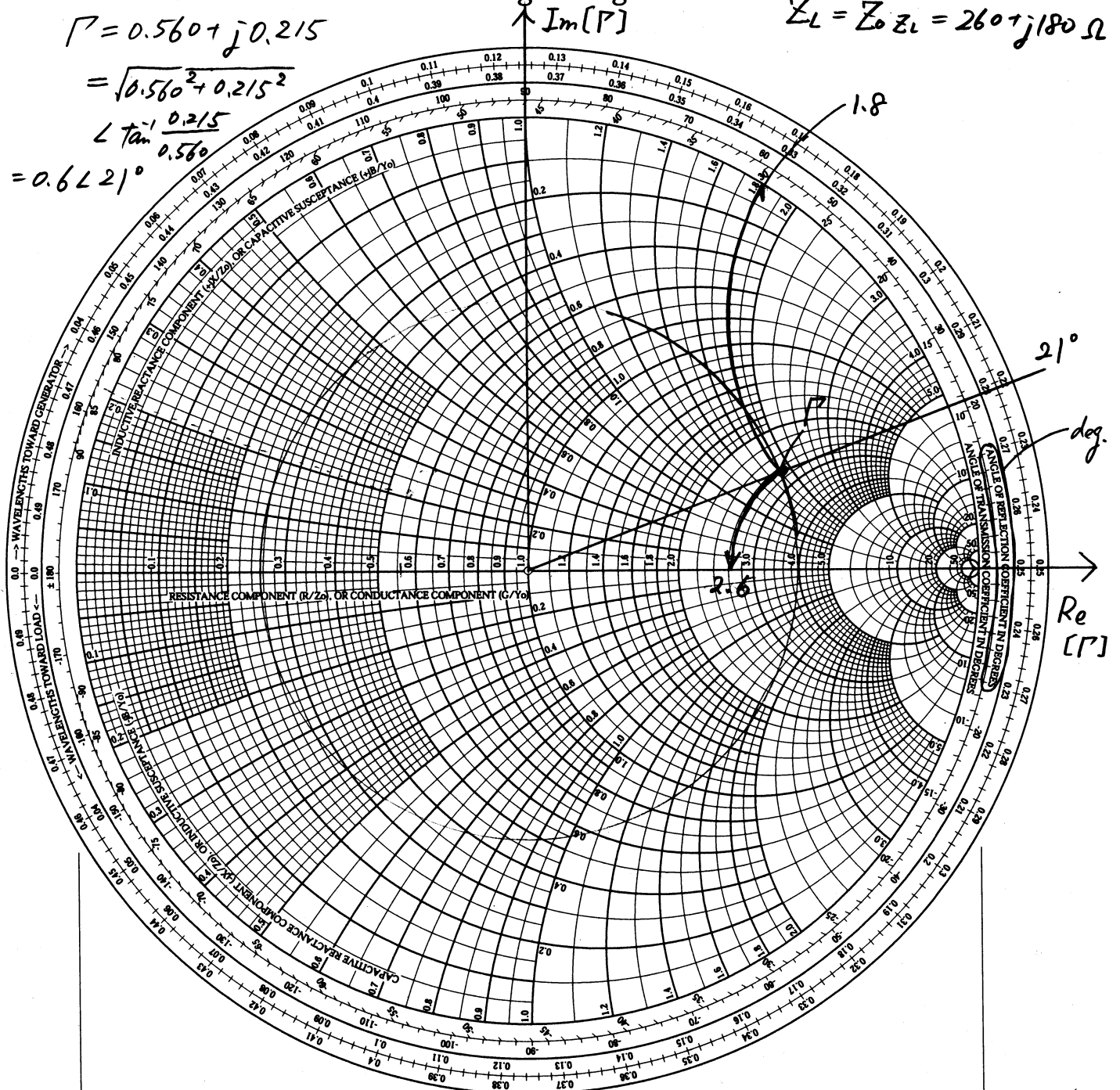


Voltage reflection coeff.  $\Gamma$   
 (Current)

# The Complete Smith Chart

Black Magic Design

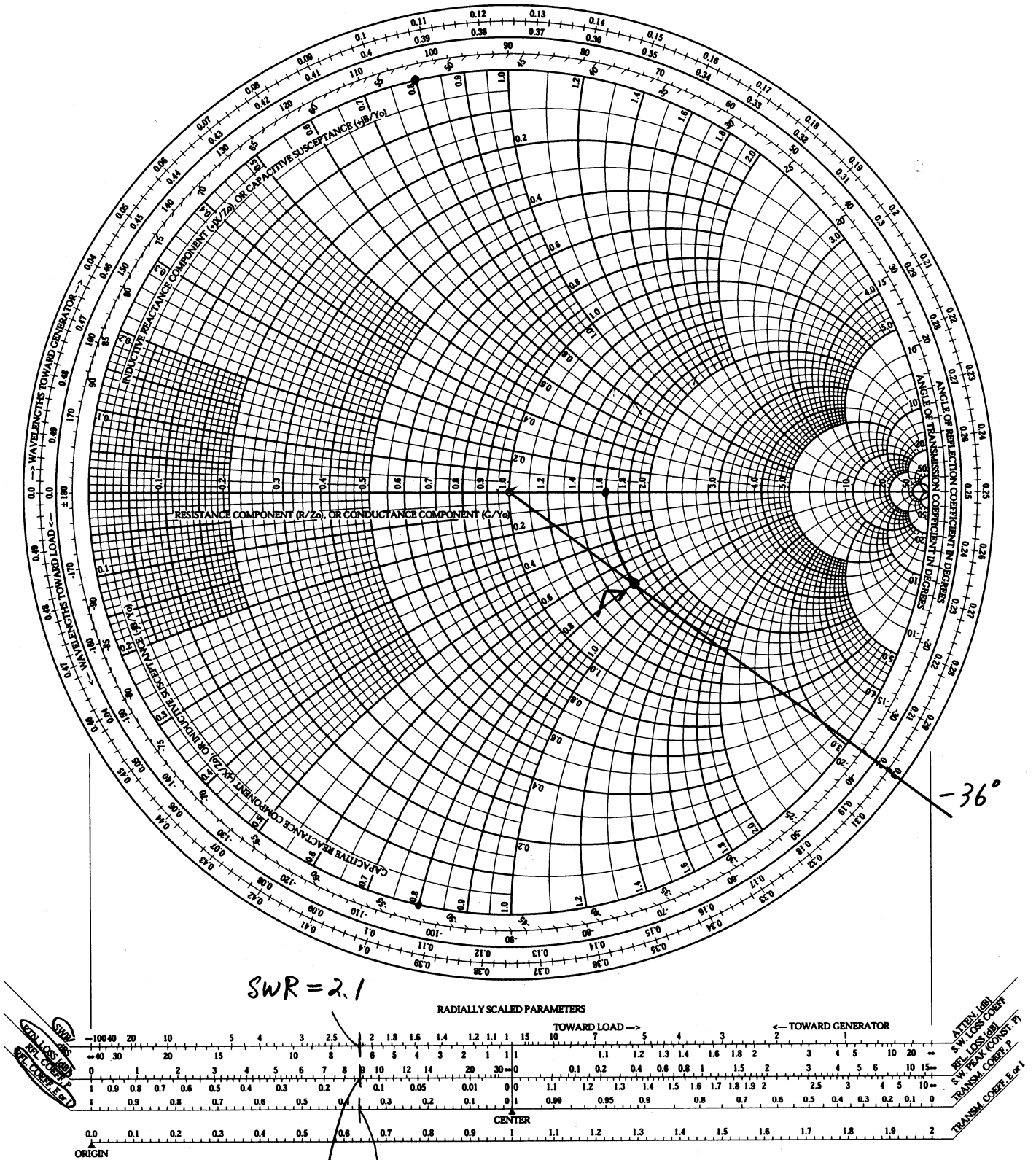

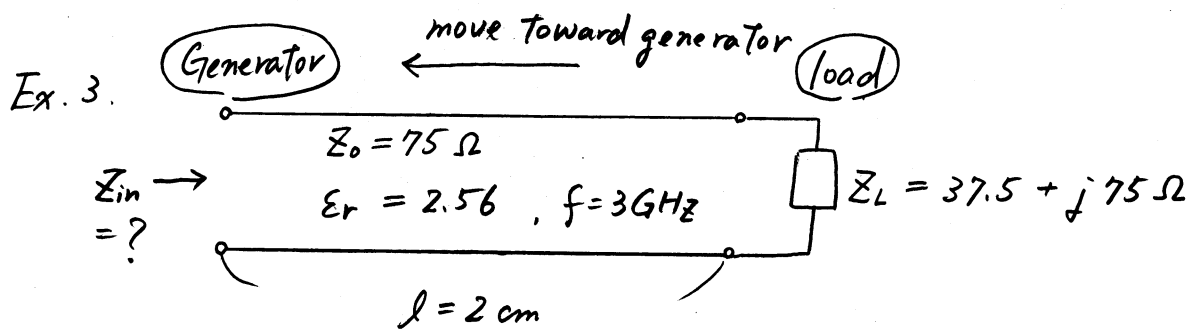ATTEN: (dB)  
 SW LOSS COEFF  
 RETN LOSS (dB)  
 TRANSM COEFF P  
 TRANSM COEFF E



$$SWR = ?$$

Ans.  $\Gamma = \frac{Z_L}{Z_0} = 0.5 + j1$

At 3 GHz with  $\epsilon_r = 2.56$ ,

$$\lambda = \frac{c_0}{\sqrt{\epsilon_r} f} = \frac{3 \times 10^8}{\sqrt{2.56} \cdot 3 \times 10^9} = 0.0625 \text{ m}$$

$$l = 2 \text{ cm} = 0.32 \lambda$$

plot.

move toward generator.

$$Z_{in} = 0.25 - j0.27$$


$$Z_{in} = Z_0 Z_{in} = 75(0.25 - j0.27) = 18.75 - j20.25 \Omega$$

$$SWR \sim 4.2 \text{ (from scale)}$$


Ex. 3.

# The Complete Smith Chart

## Black Magic Design

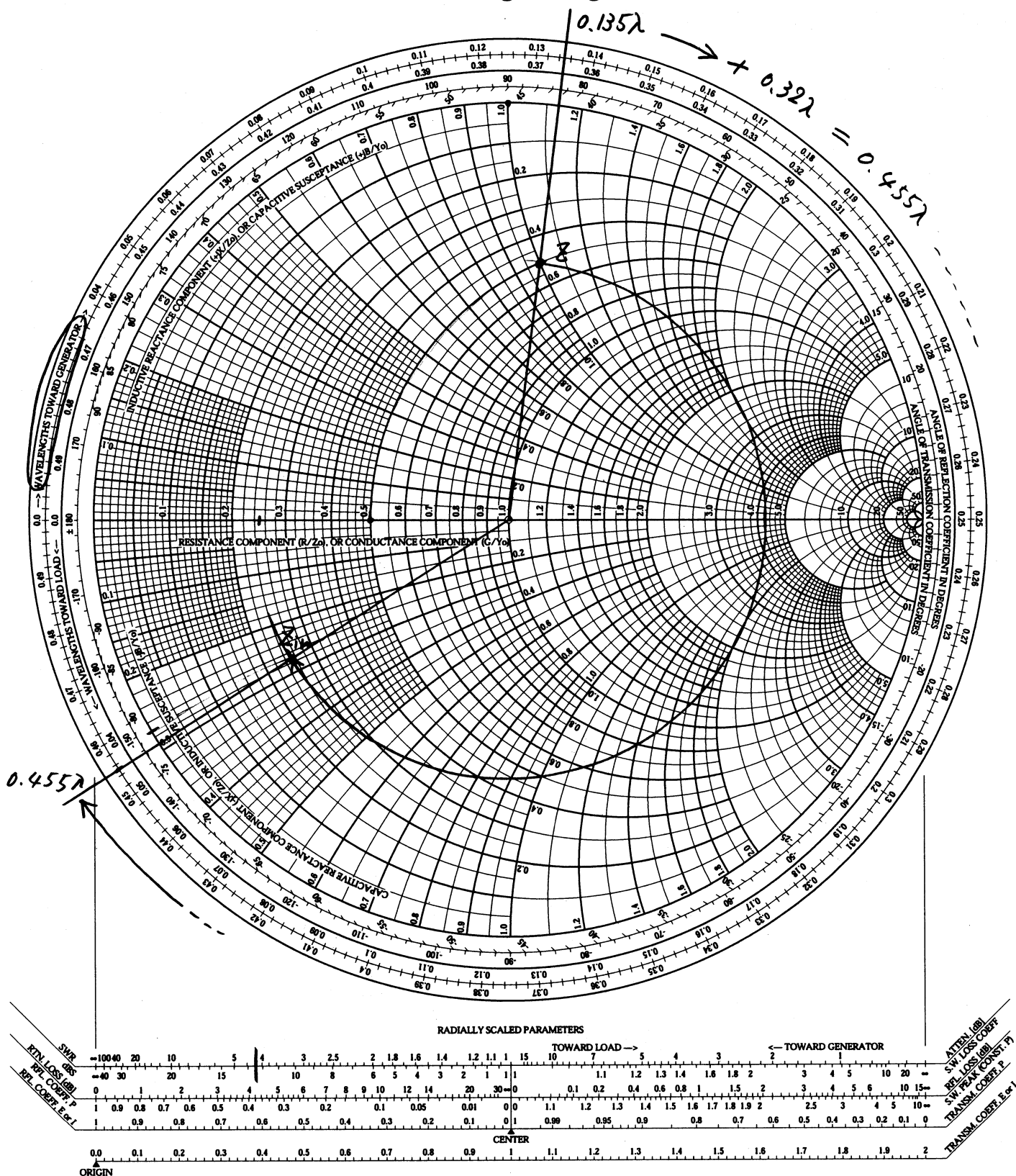

Ex. 4

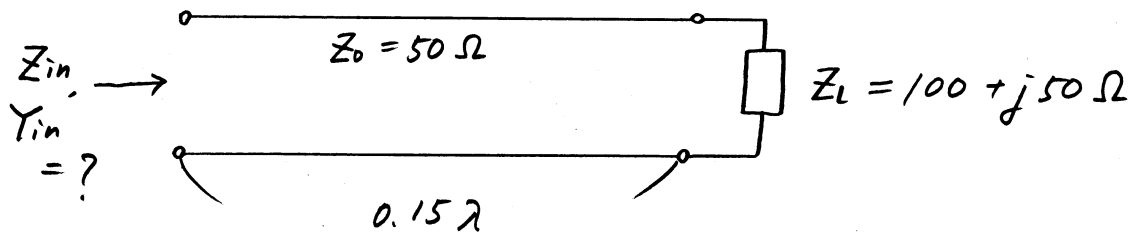

Ans.  $Z_L = \frac{Z_L}{Z_0} = 2 + j1$

↓ plot.

move toward generator by  $0.15\lambda$

↓  
 $Z_{in} = 0.75 - j0.81$

$Z_{in} = Z_0 Z_{in} = 37.5 - j40.5 \Omega$

superimpose the admittance chart and read that

$y_{in} = 0.62 + j0.67$

↑  
attention!

$Y_{in} = Y_0 y_{in} = \frac{1}{Z_0} y_{in} = \frac{0.62 + j0.67}{50}$

$= 0.0124 + j0.0134 \text{ S}$




Ex. 4


impedance scale

# The Complete Smith Chart

## Black Magic Design

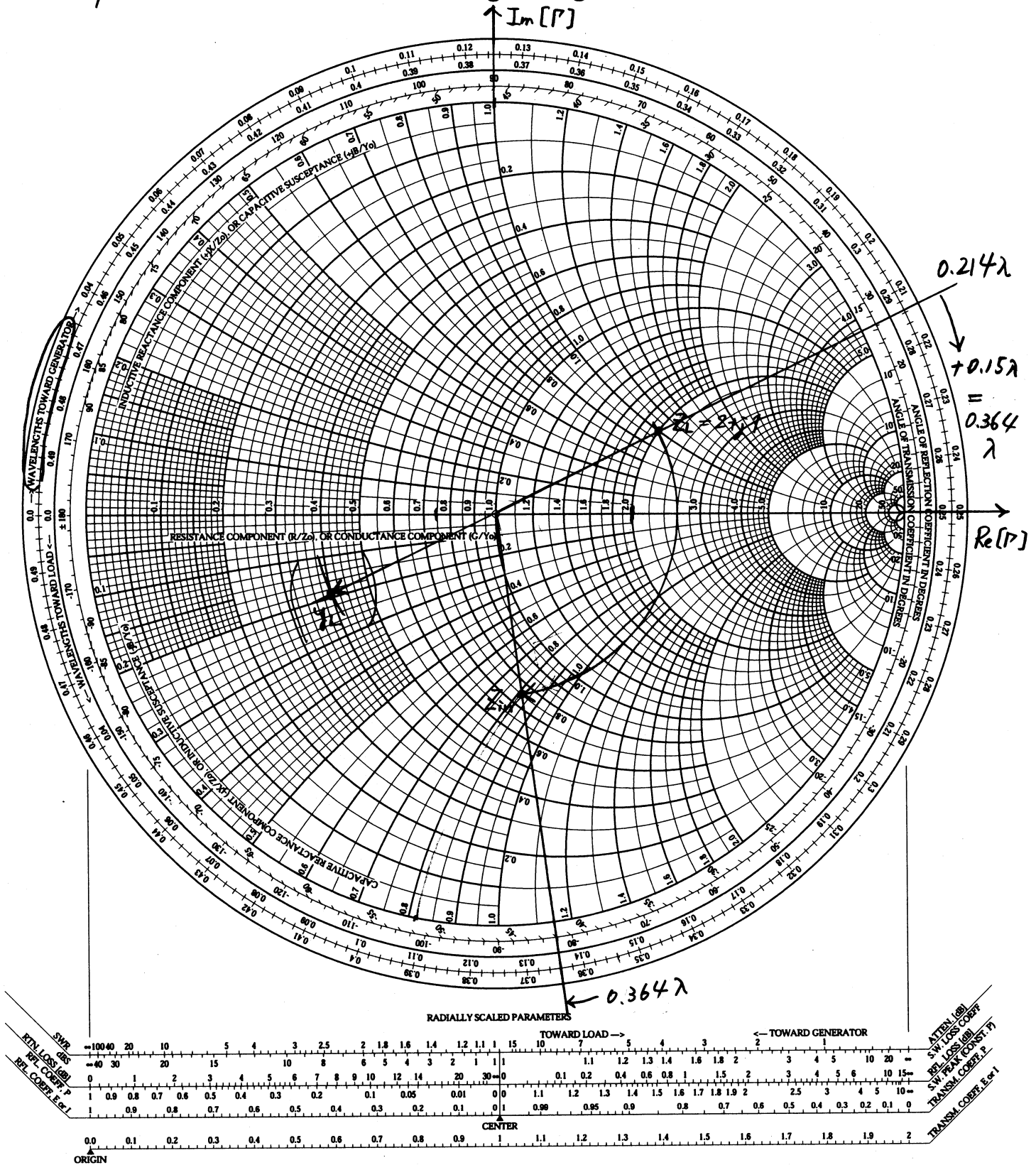

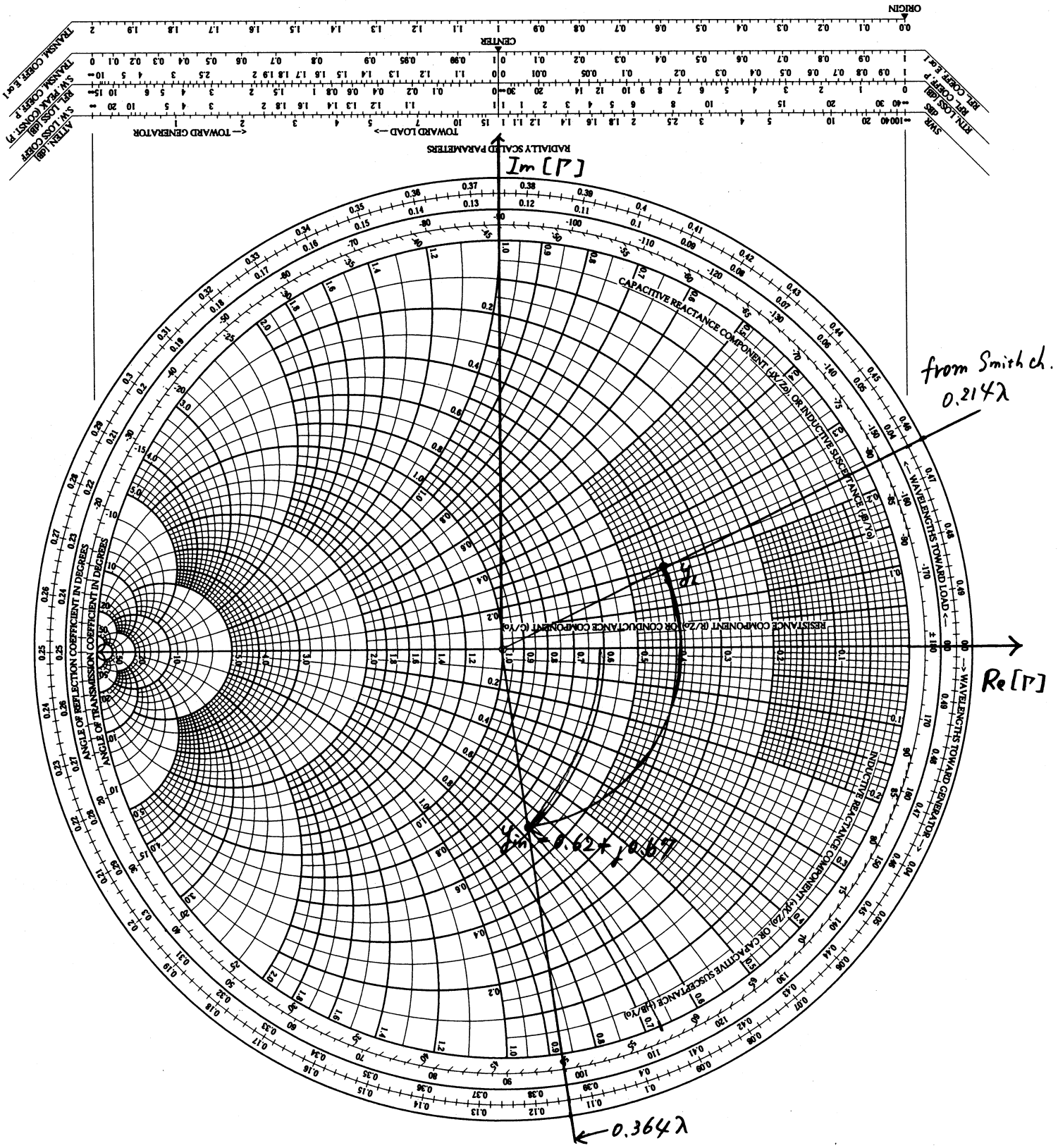Ex. 4. admittance scale (180° rotation of impedance scale)



The Complete Smith Chart  
Black Magic Design